

Hardware Design Interview Questions And Answers Guide.



Global Guideline.

<https://globalguideline.com/>



Hardware Design Job Interview Preparation Guide.

Question # 1

Hardware Design interview questions part 1:

Answer:-

1. What are the various hardware design techniques?
2. What are passive components/
3. What are the various board design issues?
4. What are analog power supply systems?
5. What do you understand by overvoltage protection?
6. What is thermal management?
7. What is a breadboard?
8. What is the purpose of prototyping?
9. Explain the term dielectric absorption?
10. What do you understand by capacitor parasitic?

[Read More Answers.](#)

Question # 2

Hardware Design interview questions part 2:

Answer:-

11. What is the dissipation factor? How is it calculated?
12. Explain tolerance?
13. What is a potentiometer used for?
14. What are the various hardware design tools available?
15. What is a HDL?
16. How can a two input NAND gate be converted into an inverter?
17. Define set up time & hold time constraints?
18. Draw a circuit to divide the clock frequency by half.
19. Design a divide-by-3 sequential circuit with 50% duty circle.
20. What are adder circuits explain?

[Read More Answers.](#)

Question # 3

Hardware Design interview questions part 3:

Answer:-

21. Give the truth table of a half-adder?
22. What are transmission gates?
23. What do you understand by DFT?
24. What are fault models?
25. Explain scan technologies
26. Explain BST?
27. What are the differences between BST and BIST?
28. State the differences between LFSR and MISR?
29. What is IDDQ?
30. What do you understand by the term recovery design?

[Read More Answers.](#)

Question # 4

Hardware Design interview questions part 4:

Answer:-

31. What are data flow diagrams?
32. What are compilers?
33. Explain the functioning of compilers.
34. What are microcontrollers?



35. Explain the functioning of microcontrollers.
36. What is assembly language?
37. What do you understand by interrupt latency?
38. Explain RTOS.
39. How does a binary counter works?
40. What are the numbers of bit combinations in a byte?

[Read More Answers.](#)

Question # 5

Hardware Design interview questions part 5:

Answer:-

41. What is equivalence checking?
42. What is the Moores law?
43. What is the difference between simulation and emulation?
44. What is the use of RTL?
45. State the differences between VHDL and Verilog?
46. What do you understand by synthesis?
47. Explain the bottom-up design process.
48. What are synchronous circuits?
49. How can distorted signals be identified with the use of SNR?
50. What are the various practices for improving SNR?

[Read More Answers.](#)

Question # 6

How to design a divide-by-3 sequential circuit with 50% duty circle?

Answer:-

take a counter with 3 f/f's that is to say with 6 states(2^3) now double the i/p clock frequency to the counter the o/p of the 3rd f/f is divide by 6 of the i/p with 50% duty cycle so effectively u got divide by 3 freq with 50% duty cycle.

[Read More Answers.](#)

Question # 7

Which are the two ways of converting a two input NAND gate to an inverter?

Answer:-

Short the two inputs of the nand gate and give the same input to the common wire, the nand gate works as an inverter. One way is shorting the two inputs of the NAND gate and passing the input.

truth table:

A	B	output
1	1	0
0	0	1

The second way is passing the input to only one input(say A) of the NAND gate. Since the other input(say B) is floating, it is always logic one.

truth table:

A	B	output
1	1	0
0	1	1

[Read More Answers.](#)

Question # 8

How to detect sequence of "1101" arriving serially from signal line?

Answer:-

Sequence detector : A sequence detector gives an output of 1 on detecting the given sequence else the output is zero.

Ex : if the given sequence to be detected is 111
and input stream is 1 1 0 1 1 1 0 0 1 0 1 1 1 1 1
the output should be 0 0 0 0 0 1 0 0 0 0 0 0 1 1 1.

Soln:

One of the different possible ways to detect a sequence is using a Mealy type FSM.

Using the following table the State machine can be designed.

[Read More Answers.](#)

Question # 9

Explain what is Transmission Gate-based D-Latch?

Answer:-

The Transmission-Gate input is connected to the D_LATCH data input (D), the control input to the Transmission-Gate is connected to the D_LATCH enable input (EN) and the Transmission-Gate output is the D_LATCH output (Q).

[Read More Answers.](#)

Question # 10

Draw a Transmission Gate-based D-Latch?

Answer:-

The Transmission-Gate's input is connected to the D_LATCH data input (D), the control input to the Transmission-Gate is connected to the D_LATCH enable input



(EN) and the Transmission-Gate output is the D_LATCH output (Q)

[Read More Answers.](#)

Question # 11

Suppose you have a combinational circuit between two registers driven by a clock. What will you do if the delay of the combinational circuit is greater than your clock signal?

Answer:-

Use the concept of register-retiming.
divide the total combinatorial delay in two segments such that individually the delay is less the clock period.
this can be done by inserting a flip-flop in the combinational path.

e.g.
clock period --- 5 ns
total cominational delay ---- 7
then divide the 7ns path in two path of 4 or 3 (best results are obtained if delays are same for both path i.e 3.5ns) by inserting a flip-flop in between.

[Read More Answers.](#)

Question # 12

How do you detect a sequence of "1101" arriving serially from a signal line?

Answer:-

Sequence detector : A sequence detector gives an output of 1 on detecting the given sequence else the output is zero.

Ex : if the given sequence to be detected is 111
and input stream is 1 1 0 1 1 1 0 0 1 0 1 1 1 1 1
the output should be 0 0 0 0 0 1 0 0 0 0 0 1 1 1.

Soln:

One of the different possible ways to detect a sequence is using a Mealy type FSM.

Using the following table the State machine can be designed.

since the number of bits in the sequence 1101 is 4 we have 4 states

PS Seq detected by the state NS/output

X=0 X=1

S1 - S1/0 S2/0

S2 1 S1/0 S3/0

S3 11 S4/0 S3/0

S4 110 S1/0 S2/1

when in state S4 (PS),and input(X) from the sequence is 1,the sequence "1101" has been detected once and (to find the next state select the longest "seq identified by a state" column that matches part of the sequence 1101--ie.,1 or 01 or 101)the NS is S2 since the sequence detected by the state S2 is 1(in 1101- 01 or 101 ,etc are not present in the seq identified by the state column .)

[Read More Answers.](#)

Question # 13

Give the truth table for a Half Adder. Give a gate level implementation of the same.

Answer:-

TRUTH TABLE FOR HALF ADDER:

A B SUM CARRY

0 0 0

0 1 1 0

1 0 1 0

1 1 0 1

IMPLEMENTATION:

For SUM, The two inputs A and B are given to XOR gate.

For Carry, The two inputs A and B are given to AND gate.

[Read More Answers.](#)

Question # 14

Design a divide-by-3 sequential circuit with 50% duty circle.

Answer:-

Take a smiths counter with 3 f/f's

that is to say with 6 states(2*3)

now double the i/p clock frequency to the counter

the o/p of the 3rd f/f is divide by 6 of the i/p with 50% duty cycle

so effectively u got divide by 3 freq with 50% duty cycle

[Read More Answers.](#)

Question # 15

Give two ways of converting a two input NAND gate to an inverter.



Answer:-

One way is shorting the two inputs of the NAND gate and passing the input.

truth table:

A B output

1 1 0

0 0 1

The second way is passing the input to only one input(say A) of the NAND gate. Since the other input(say B) is floating, it is always logic one.

truth table:

A B output

1 1 0

0 1 1

[Read More Answers.](#)

Question # 16

How do you detect if two 8-bit signals are same?

Answer:-

XOR each bits of A with B (for eg A[0] xor B[0]) and so on. the o/p of 8 xor gates are then given as i/p to an 8-i/p nor gate. if o/p is 1 then A=B.

[Read More Answers.](#)

Question # 17

Give a circuit to divide frequency of clock cycle by two?

Answer:-

You can divide the frequency of a clock by just implementing T Flip flop.

Give clock as clock input and tie the T input to logic 1.

[Read More Answers.](#)

Question # 18

What are set up time & hold time constraints? What do they signify? Which one is critical for estimating maximum clock frequency of a circuit?

Answer:-

Suppose your flip-flop is positive edge triggered. time for which data should be stable prior to positive edge clock is called setup time constraint .

Time for which data should be stable after the positive edge of clock is called as hold time constraint.

if any of these constraints are violated then flip-flop will enter in meta stable state, in which we cannot determine the output of flip-flop.

there are two equation:

1. $T_{cq} + T_{comb} > T_{skew} + T_{hold}$

2. $T_{cq} + T_{comb} < T_{skew} + T - T_{setup}$

T_{cq} is time delay when data enters the flip-flop and data comes at output of flip flop.

T_{comb} is the logic delay between two flip flop.

T_{skew} is the delay of clock to flip flop: suppose there are two flip flop ,if clock reaches first to source flip flop and then after some delay to destination flip flop ,it is positive skew and if vice versa then negative skew.

so if you take 2 eq you will see that setup time is the determining factor of clock's time period.

[Read More Answers.](#)

Question # 19

What are the different Adder circuits you studied?

Answer:-

Adders are generally of five types:

1) Ripple Carry Adder:

The Ripple carry adder(RCA) consists of a building block named Half Adder(HA) which is cascaded to form a Full Adder(FA). These building blocks HAs and FAs are also the building blocks of all types of adders. The n full adders are cascaded to form n bit RCA.

The full adder has three input pins(input A_i ,input B_i ,carryin C_i) and two output pins(Sum and C_{i+1}).Its equations are:

$Sum = A_i \oplus B_i \oplus C_i$

$C_{i+1} = A_i \cdot B_i + B_i \cdot C_i + A_i \cdot C_i$

2)Carry Lookahead Adder:

The Carry Lookahead Adder(CLA) reduces the delay as that in RCA. Let $G_i = A_i \cdot B_i$, and $P_i = A_i \oplus B_i$, then $C_{i+1} = G_i + P_i \cdot C_i$.

The expressions for Sum and C_{i+1} is then defined completely in terms of input pins rather wait for input carry to appear.

3)Carry Select Adder:

The carry select adder uses duplicate modules for each combination of input carry(i.e. 1 and 0).The multiplexers then select the appropriate sum and carry output according to the carry output of the preceding stages.

[Read More Answers.](#)

Question # 20

Design a state machine that produce 1 at its output z. when the specified 3 bit sequence appears at its input x unless the specified 3 bit sequence 2 occur this should then disable the out put until the circuit restarted. sequence1 001 and sequence 2 011?



Answer:-

No Answer is Posted For this Question

Be the First to [Post Your Answer Now.](#)

Global Guideline - COM

Computer Hardware Most Popular Interview Topics.

- 1 : [Basic Computer Frequently Asked Interview Questions and Answers Guide.](#)
- 2 : [A + \(Plus\) Hardware Frequently Asked Interview Questions and Answers Guide.](#)
- 3 : [Computer Architecture Frequently Asked Interview Questions and Answers Guide.](#)
- 4 : [Electronics Frequently Asked Interview Questions and Answers Guide.](#)
- 5 : [Microprocessor Frequently Asked Interview Questions and Answers Guide.](#)
- 6 : [Embedded System Frequently Asked Interview Questions and Answers Guide.](#)
- 7 : [Motherboard Frequently Asked Interview Questions and Answers Guide.](#)
- 8 : [Basic Input Output System Frequently Asked Interview Questions and Answers Guide.](#)
- 9 : [8085 Frequently Asked Interview Questions and Answers Guide.](#)
- 10 : [Central Processing Unit \(CPU\) Frequently Asked Interview Questions and Answers Guide.](#)

About Global Guideline.

Global Guideline is a platform to develop your own skills with thousands of job interview questions and web tutorials for fresher's and experienced candidates. These interview questions and web tutorials will help you strengthen your technical skills, prepare for the interviews and quickly revise the concepts. Global Guideline invite you to unlock your potentials with thousands of [Interview Questions with Answers](#) and much more. Learn the most common technologies at Global Guideline. We will help you to explore the resources of the World Wide Web and develop your own skills from the basics to the advanced. Here you will learn anything quite easily and you will really enjoy while learning. Global Guideline will help you to become a professional and Expert, well prepared for the future.

* This PDF was generated from <https://GlobalGuideline.com> at **November 29th, 2023**

* If any answer or question is incorrect or inappropriate or you have correct answer or you found any problem in this document then don't hesitate feel free and [e-mail us](#) we will fix it.

You can follow us on FaceBook for latest Jobs, Updates and other interviews material.
www.facebook.com/InterviewQuestionsAnswers

Follow us on Twitter for latest Jobs and interview preparation guides
<https://twitter.com/InterviewGuide>

Best Of Luck.

Global Guideline Team
<https://GlobalGuideline.com>
Info@globalguideline.com